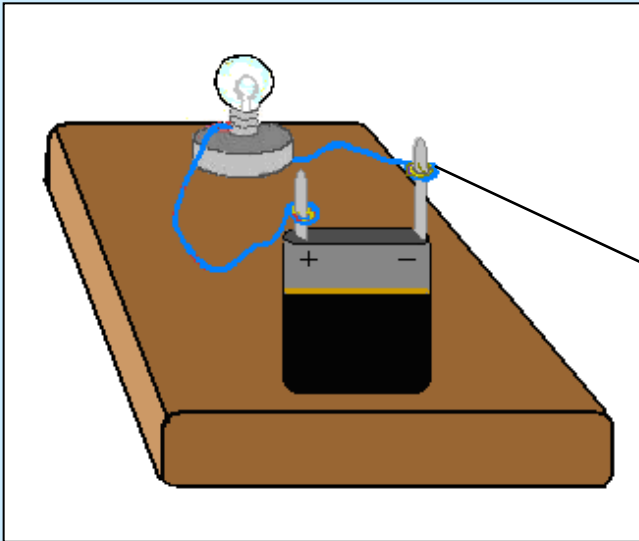


Activity 13 : Conductive, non-conductive...



The lamp is in good condition
The battery is in good condition
They are well connected, the circuit is closed.

The lamp does not work!

Not all wires allow the electric current to pass through: some materials do not conduct electricity.

Complete the circuit with the appropriate equipment so that the bulb will light up...

