

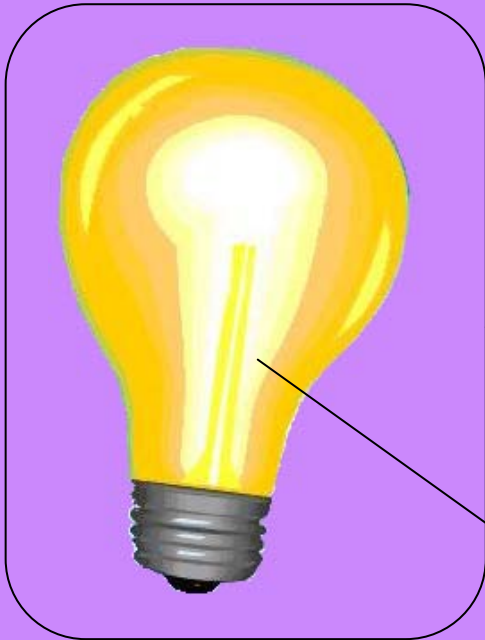


Activity 12 : Electricity

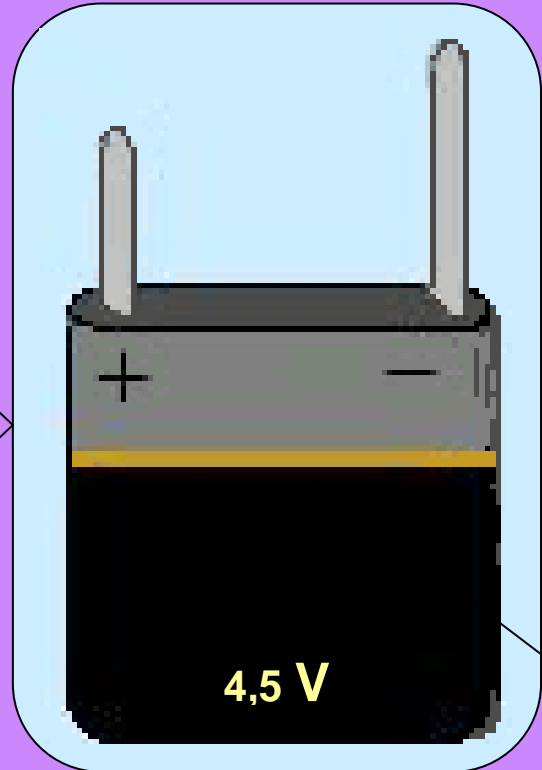


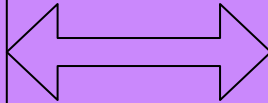The electric lamp is in good condition when the filament is not broken.




The battery provides power.

Open circuit, closed circuit...

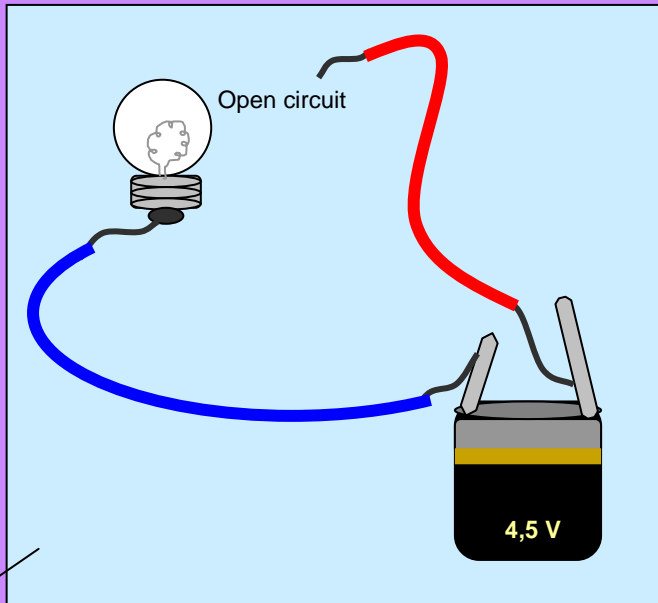

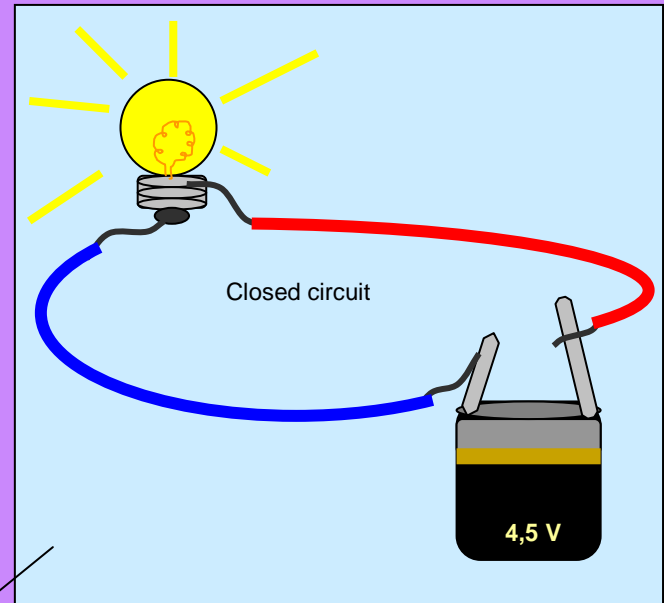The path through which the electric current circulates is cut. If the electric circuit is cut (open) the lamp is not fed. It is switched off.



The electric circuit is not cut. It is closed. The lamp is fed. It is switched on.