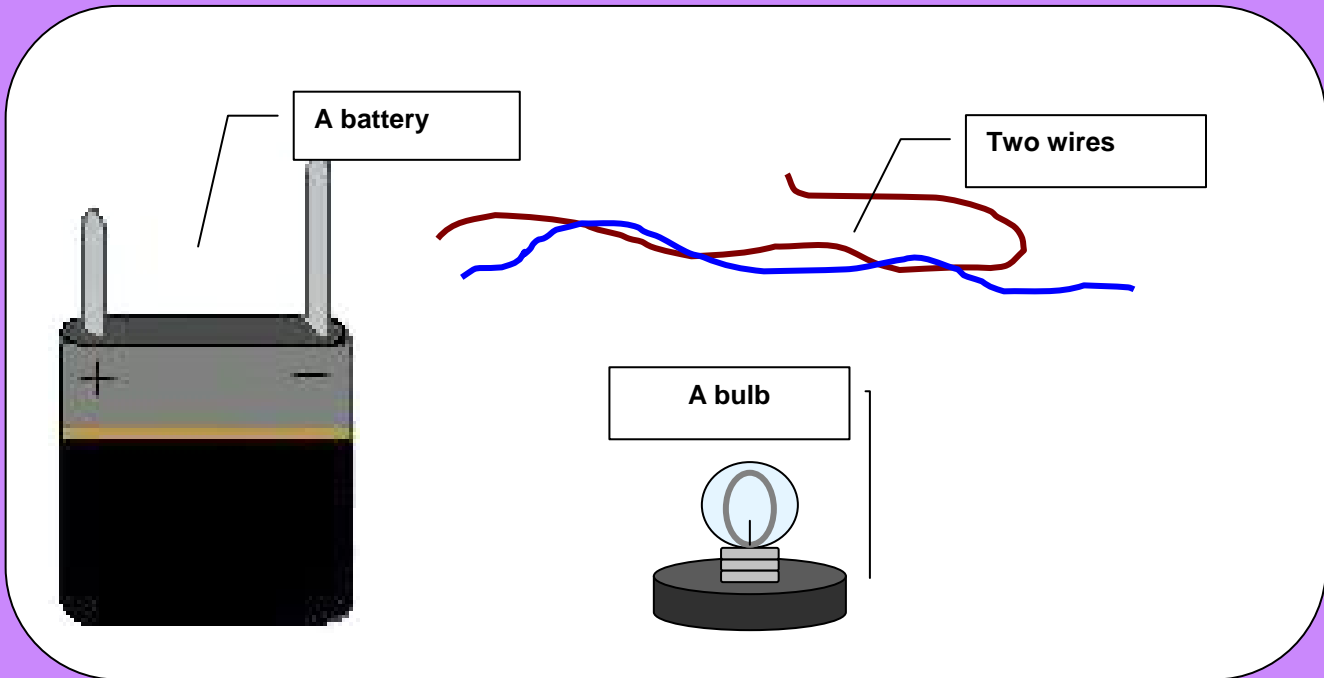
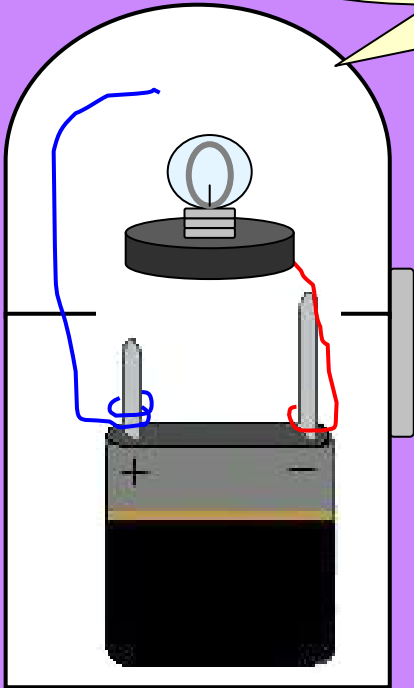


Activity 16 : To build a torch you need...



- Check that :
- the bulb is not burned out
 - the battery is not flat
 - the two wires are conductors (in metal)



To light up the bulb, the circuit must be closed.

